

NORTHWESTERN UNIVERSITY
Department of Electrical and Computer Engineering

ECE-221 Fundamentals of Circuits

LAB 3: FIRST-ORDER TRANSIENT RESPONSES

Part A: First order transient response

A1. Transient Response of a Series RC Circuit

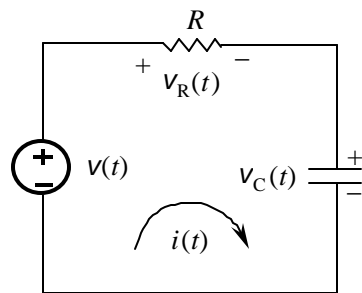


Figure 1

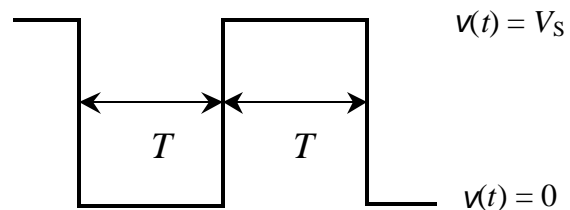


Figure 2

Theory

Consider the series RC circuit of Fig. 1. We will first determine a linear first-order differential equation describing $v_C(t)$ of the form

$$\dot{x}(t) + Px(t) = Q(t)$$

and then solve it by way of the integrating factor method. If we multiply both sides of this equation by

$$e^{\int P dt} = e^{Pt}$$

and make use of the product rule

$$\frac{d}{dt}(e^{Pt} x(t)) = e^{Pt} \dot{x}(t) + P e^{Pt} x(t)$$

we obtain the following expression

$$d(e^{Pt} x(t)) = e^{Pt} Q(t) dt$$

After taking the indefinite integral of both sides,

$$e^{Pt} x(t) = \int e^{Pt} Q(t) dt + K$$

we obtain an algebraic expression for $x(t)$ in terms of a general forcing function $Q(t)$ (assuming we can perform the necessary integration).

- 1.1) Write down the following equations: a KVL equation relating $v(t)$, $v_R(t)$, and $v_C(t)$; Ohm's law for the resistor, and a differential equation relating $v_C(t)$ and the loop current $i(t)$.
- 1.2) Combine the above equations to obtain a linear, first-order differential equation for $v_C(t)$ in terms of $v(t)$, R , and C .
- 1.3) Use the integrating factor method to produce an expression for $v_C(t)$ in terms of R , C , and a general forcing function $v(t)$. Show all your work.
- 1.4) Let $v(t) = V_S u(t)$, where $u(t)$ is the unit step function. Evaluate your expression for $v_C(t)$ under this special case. Use KVL to determine an expression for $v_R(t)$.

Procedure

We will now compare the theoretical step response of an ideal RC circuit with that measured on a real circuit, which is not ideal. Design a circuit like that of Fig. 1 to have a time constant of 0.1ms. Because we do not have a source that produces the unit step function, we will drive the circuit with the unipolar square wave of Fig. 2. Choose values for $V_S = 5\text{V}$ and $T = 0.2\text{ms}$. Set the function generator to produce a square wave as in Fig. 2, and connect it to the circuit. Observe $v_R(t)$, and $v_C(t)$ and record 10 points in the time scale to produce a graph of each of them over one period of the input.

- 1.5) Plot $v_R(t)$ and $v_C(t)$. Each plot should show the theoretical and measured waveforms on the same set of axes. List all the possible sources of discrepancy between your theoretical and measured results.
- 1.6) Is the time constant of your real circuit equal to 0.1ms? If not, is the time constant less than or greater than this value?
- 1.7) Does $v(t) = v_R(t) + v_C(t)$ for the real circuit? Is the error significant?

A2. Transient Response of a First-Order RC Filter

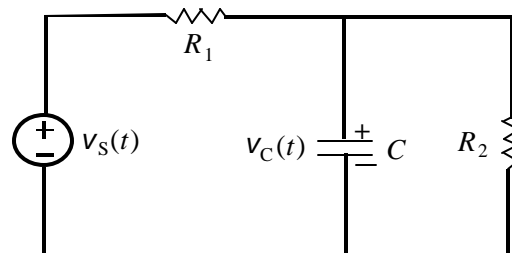


Figure 3

Theory

- 2.1) Now consider the circuit of Fig. 3. Write down a linear first-order differential equation for $v_C(t)$ in terms of R_1 , R_2 , C , and $v(t)$.

- 2.2) Obtain an expression for $v_C(t)$ in terms of R_1 , R_2 , C , and a general forcing function $v(t)$. Show all your work.
- 2.3) Again let $v(t) = V_S u(t)$. Evaluate your expression for $v_C(t)$ for this special case.

Procedure

Again we will compare theory with practice. Design a circuit like that of Fig. 3 to have a time constant of 0.1ms. Choose values for amplitude $V_S = 5V$ and $T = 0.2ms$, set the function generator to produce a square wave as in Fig. 2, and connect it to the circuit. Observe the capacitor voltage waveform, and record 10 points in the time scale to produce a graph over one period of the input.

- 2.4) Plot the theoretical and measured waveforms for $v_C(t)$ on the same set of axes.
- 2.5) Consider the capacitor voltage waveforms for each of the first two circuits. Is there more agreement between theory and practice in circuit 1 or circuit 2, or is it approximately the same?

Part B: Second order transient response

B1. Second-Order RC Filter

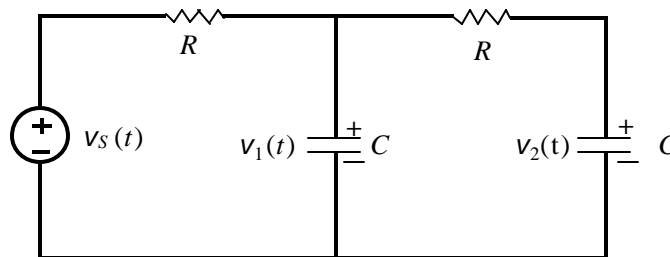


Figure 4

Theory

- 3.1) The circuit of Fig. 4 consists of two identical RC stages connected in cascade. For each of the two loops, write down two equations: one KVL, and one differential equation relating a capacitor voltage to the loop currents
- 3.2) Construct a PSpice model of this circuit and simulate a step up in voltage by using **Vpulse** as a voltage source. Measure the voltage across the second capacitor $v_2(t)$ and print out the resulting graphs. In options, choose transient from 0 to a suitable time and run the simulation with the following resistance and capacitance values:

$$R=1000\Omega \quad C=0.2\mu F$$

$$R=500\Omega \quad C=0.05\mu F$$

Procedure

Connect the circuit of Fig. 4. Use values for R, C, V_s , and T identical to those used for the circuit of Fig. 1. Observe $v_2(t)$ and collect 10 points to graph one period of the waveform.

- 3.3) Plot the theoretical waveform in PSpice and measured waveform for $v_2(t)$ in the excel spreadsheet.